

NAND2Tetris Project 3: Simulation Results

Hardware Simulator output for each chip. All simulations passed.


1. Bit

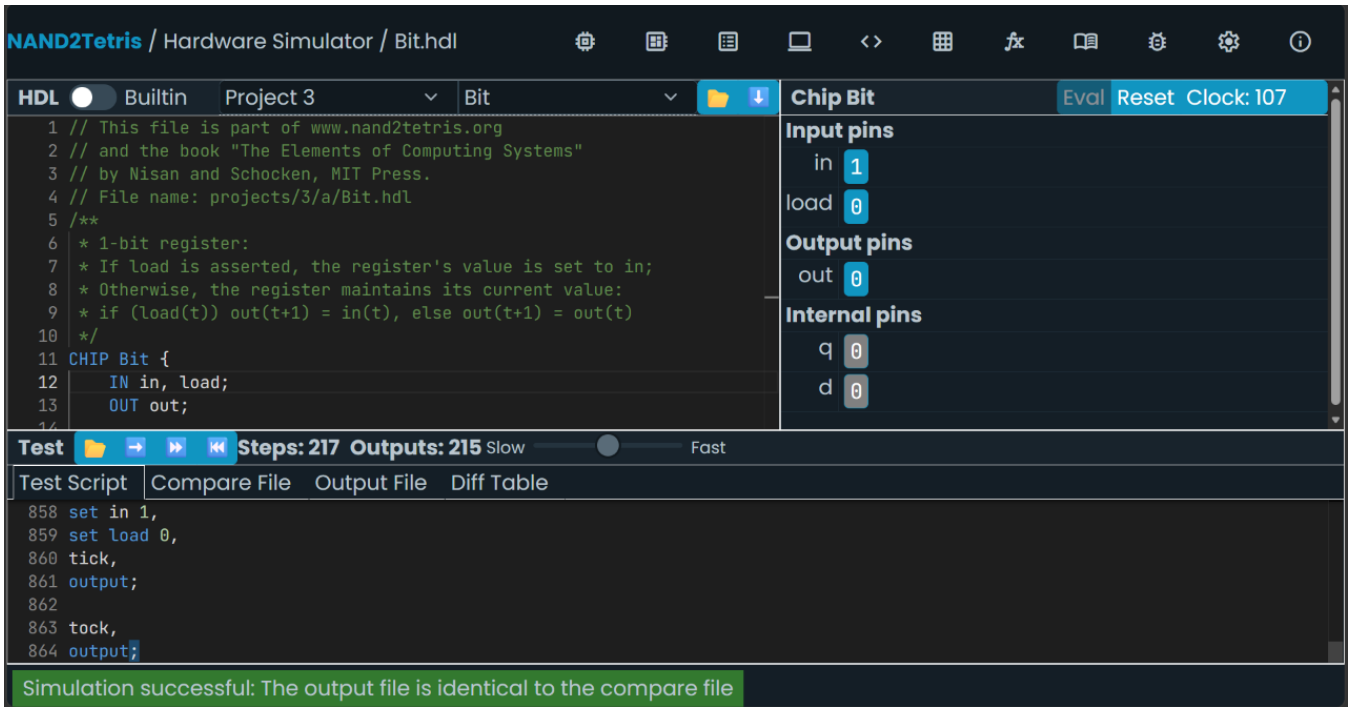


2. Register

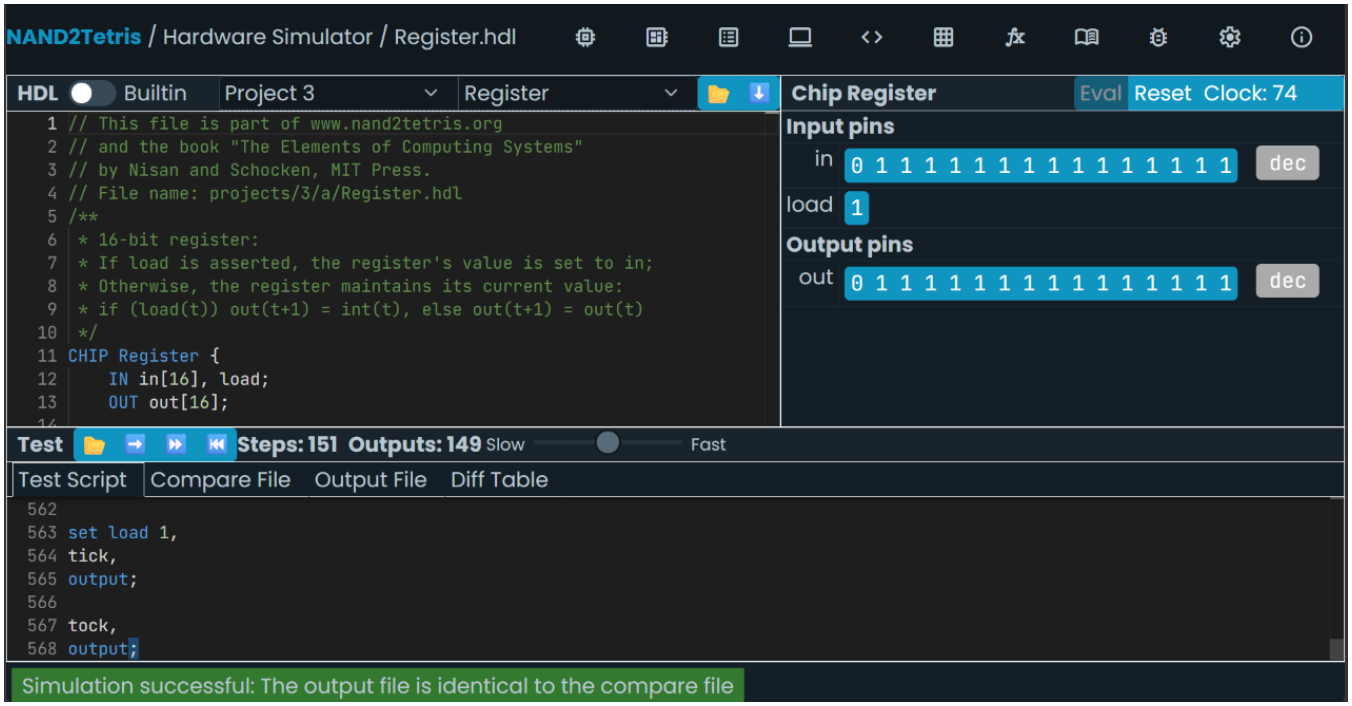


3. RAM8

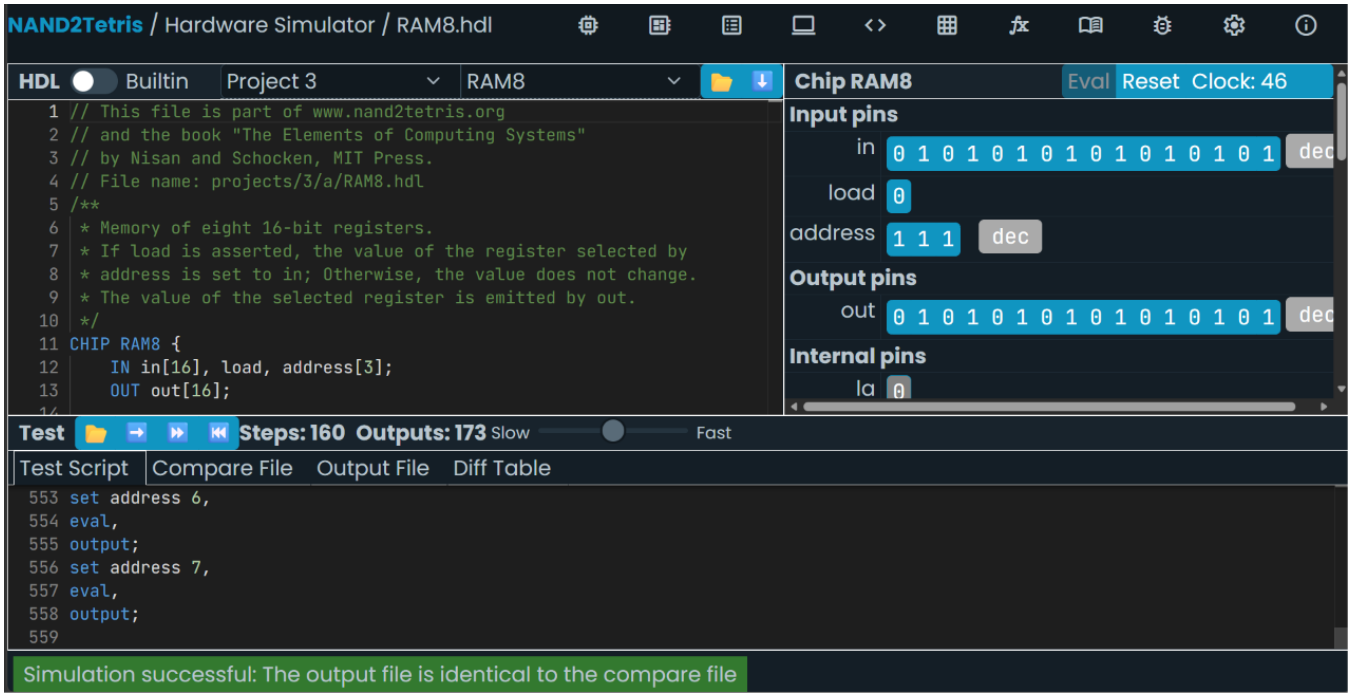


4. RAM64

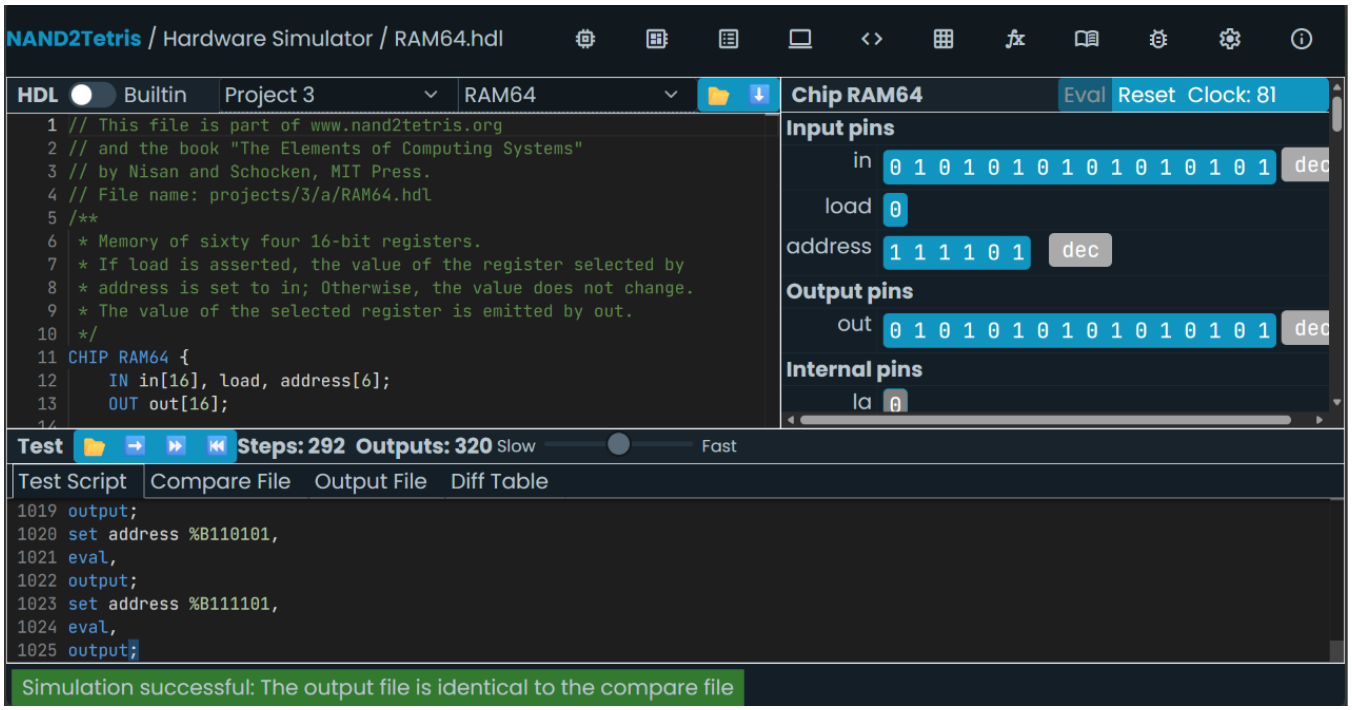


5. RAM512

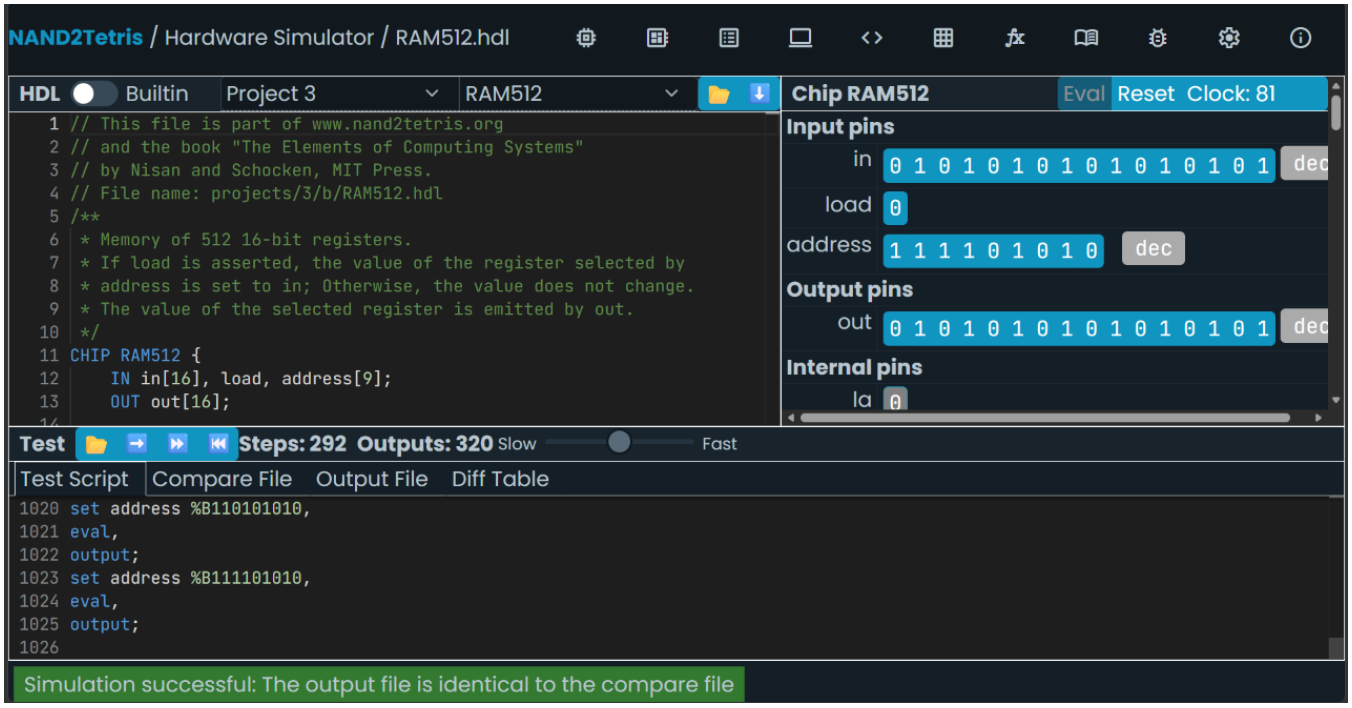


6. RAM4K

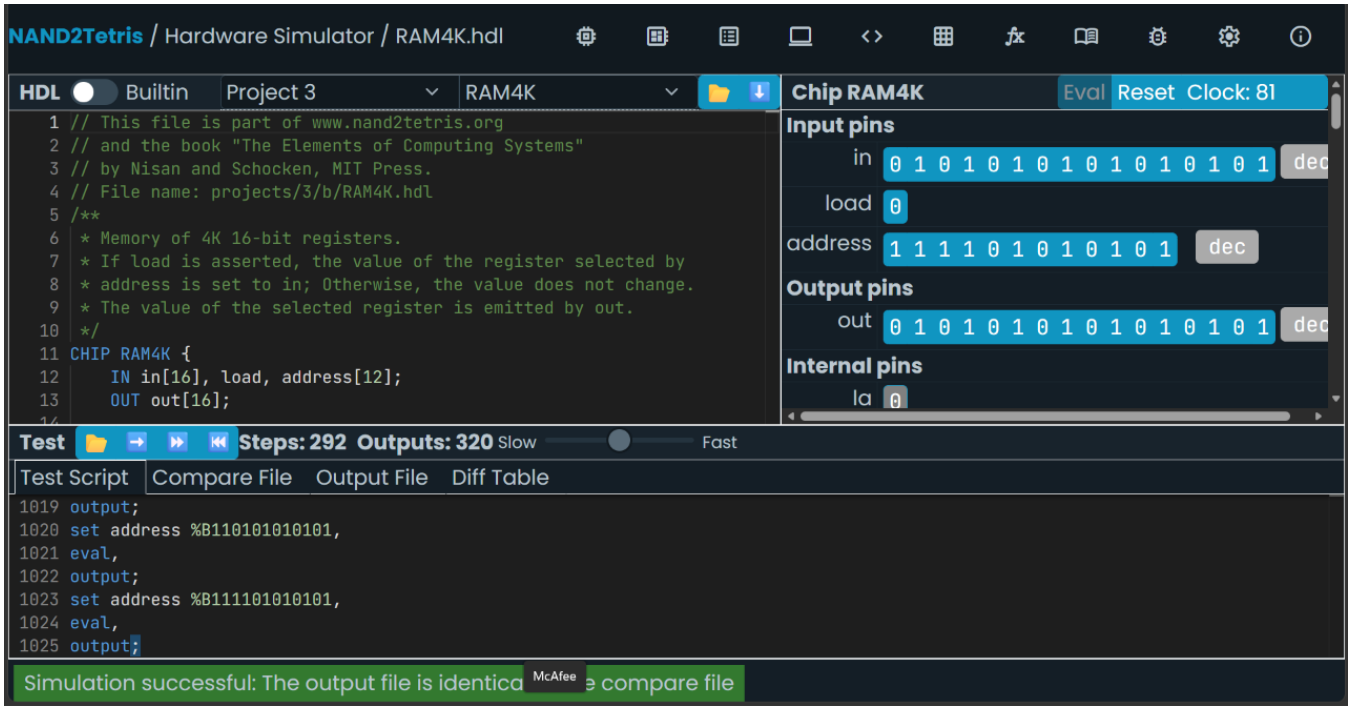

7. RAM16K

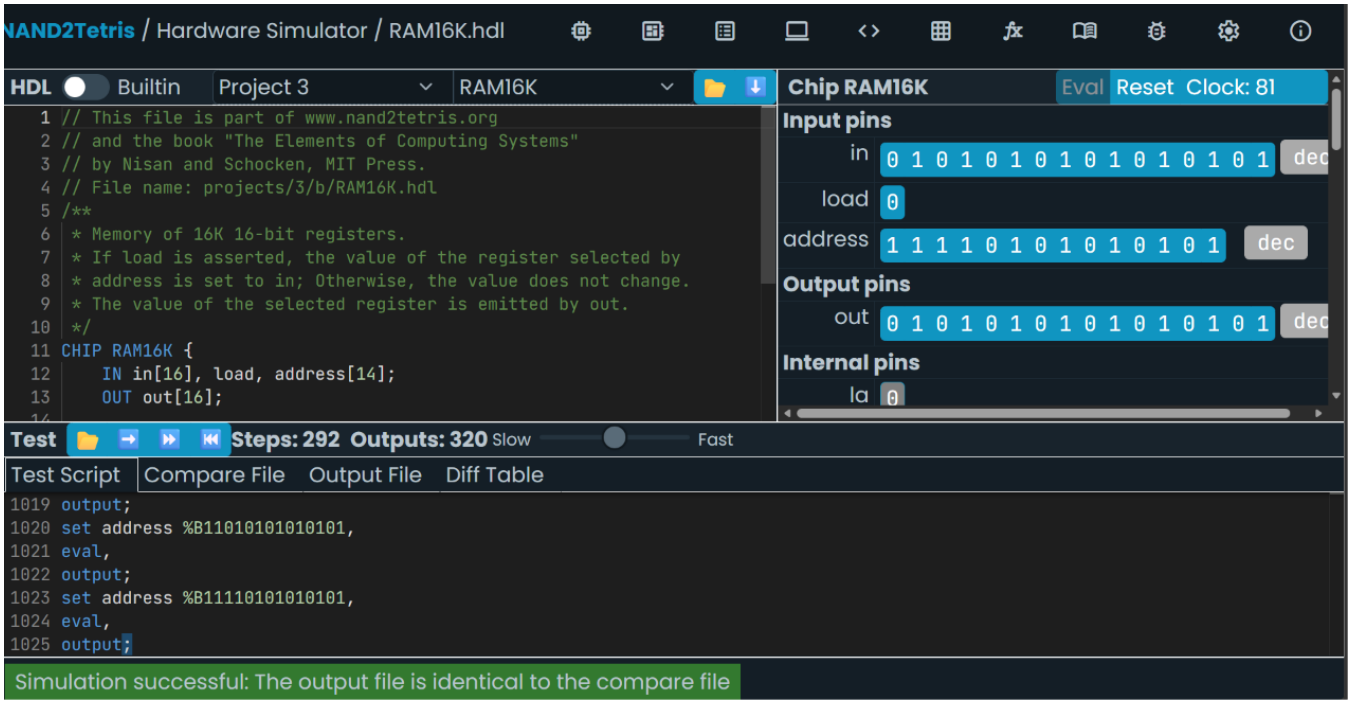

8. PC

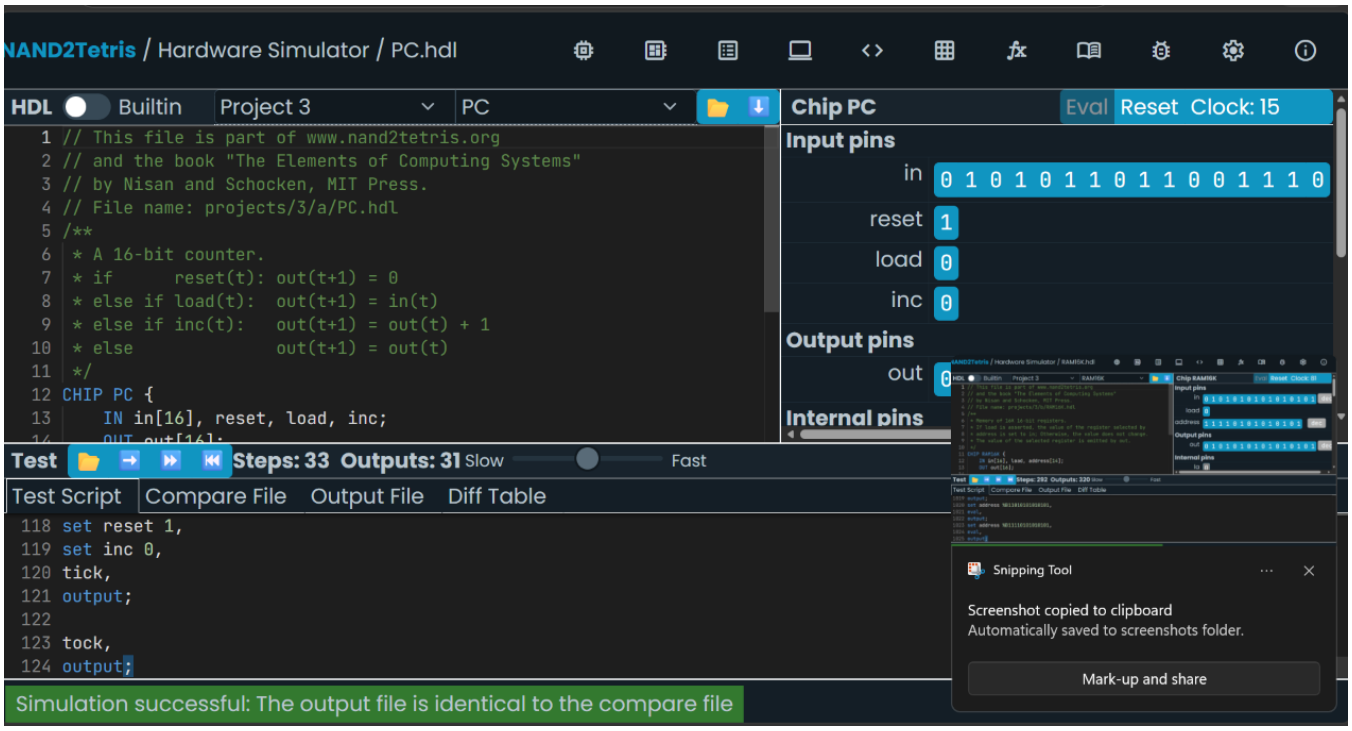

Sanchita